

Electric House Wiring Diagram

Names: _____

Description of your house:

Description of each room:

Diagram: Use the correct circuit diagram symbols to display the location and connection of ALL the wires, bulbs, batteries, and switches used to wire your house. Show the separate rooms in your diagram.

